

DSM LAB REPORT – 5

Macharla Harish

2020102062

Objective:

To build an RS latch, a JK Master-Slave Flip-Flop, and a 4-bit Up-Down Counter in Tinker cad.

Part A: SR Latch


Objective:

To Assemble a NOR latch using two NOR gates

Components Required:

- *Bread Board
- *Arduino
- *Logic Nor gates
- *Push Button
- *Led's, Resistors and connecting wires.

Reference Circuit:

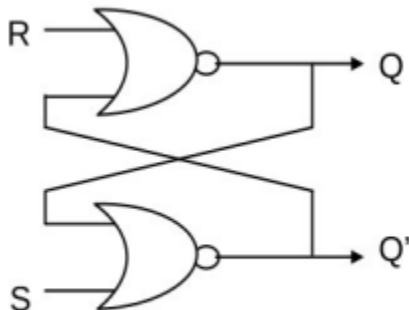

Procedure:

- 1) Construct the circuit with the components mentioned above on Bread Board as shown in the figure.
- 2) Give the inputs R and S through Arduino.
- 3) Connect the outputs Q and Q' to the Led's with resistors using connecting wires.
- 4) Note down the readings.

Observations:

| S | R | Q | Q' |
|---|---|---|----|
| 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 |

- From my observations latch works properly until both the inputs were given 1 (S=R=1) because it contradicts outputs that is the number and the complement of the number should be opposite but in this case both are equal.
- Hence it leads to forbidden state where it loses it previous states.

Link for Tinker cad:

<https://www.tinkercad.com/things/4Mij0z8XqtK-2020102062lab5part1/editel?sharecode=a2N433xRKdCb8q0q37iN1cLZkN51qa3Vxiid9V08Lqg>

Conclusion:

Truth Table for SR Latch:

Boolean exp:

$$Q(n+1) = [R + (S + Q(n))']'$$
$$= R' \cdot (Q(n) + s)$$

| S | R | Q(n+1) state |
|---|---|--------------------|
| 0 | 0 | Q(n) --> No change |
| 1 | 0 | 1 --> Set |
| 0 | 1 | 0 --> Reset |
| 1 | 1 | 0 --> Forbidden |

Part B: JK Master-Slave Flip-Flop

Objective:

To Assemble a JK Master-Slave Flip-Flop.

Components Required:

*Bread Board


*Arduino

*Logic Triple Nand gate, Two Quad Nand gates, Hex converter.

*Led's, Resistors and connecting wires.

*Push Buttons

Reference circuit:

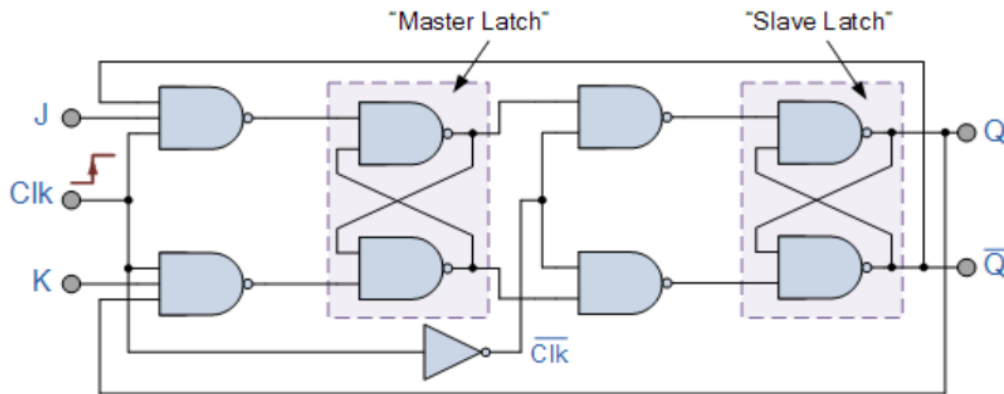

master slave JK flip flop

Procedure:

- 1) Construct the circuit with the components mentioned above on Bread Board as shown in the figure.
- 2) Give the inputs J, K and clock through Arduino.
- 3) Connect the outputs Q and Q' to the Led's with resistors using connecting wires.
- 4) Note down the readings.

Observations:

| J | K | Q | Q' |
|---|---|---|----|
| 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |
| 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

| | | | |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
|---|---|---|---|

Link for Tinker Cad:

https://www.tinkercad.com/things/dxKsmNH09wj-2020102062lab5partb/editel?sharecode=9RSBbateS7_eFFb2QpOmmggnfRt1AdkbV-rj1JOFuvl

Conclusion:

- We can theoretically understand with the behavior of the JK Master-Slave Flipflop with help of Circuit made on Tinker cad.

JK master slave flip flop function table:

| J | K | ACTION | Q_{n+1} |
|---|---|---------|-----------|
| 0 | 0 | Hold | Q_n |
| 0 | 1 | Clear | 0 |
| 1 | 0 | Set | 1 |
| 1 | 1 | Toggles | Q'_n |

Part C: 4-bit Up-Down Counter


Objective:

To study the working of a counter.

Components Required:

- *Bread Board
- *Connecting Wires, Led's and Resistors
- *Arduino

Reference Circuit:

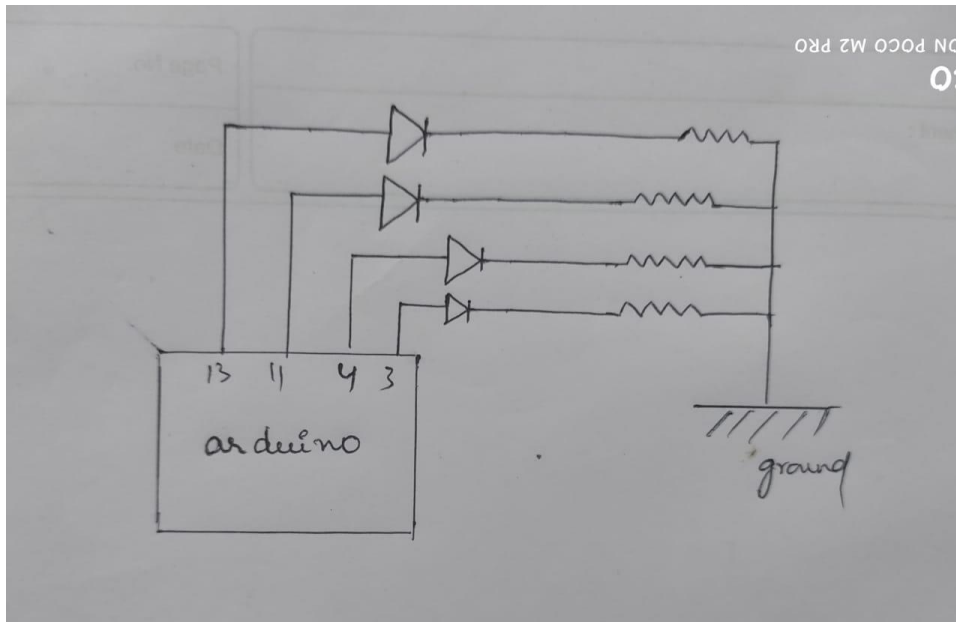

Procedure:

- Using the Timer library, implement a 4-bit counter. The bit outputs of the 4-bit ripple counter will be represented by LEDs. (One LED for each bit)
- Initialize a Timer `t` and use `t. oscillate` function to toggle the pin values in a pre-defined time period (each pin will have a different time period).
- Down counter: once the ripple counter reaches 15 (1111), make it go down to 0. You will need to stop existing timers using `t.stop`. You can use `t. every` to fire a function after a set-interval of time that will do two tasks: stop all timers and restart them in opposite direction.
- Simulate the tinkercad project and observe the LEDs.

Observations:

The ripple counter first goes UP from 0 (0000) to 15 (1111), then goes DOWN from 15 to 0, then goes UP, and this cycle repeats until the simulation is stopped.

Link for Tinkercad:

https://www.tinkercad.com/things/enbX0r9sZm2-copy-of-timer-starter-code/editel?sharecode=_aNc047fTY87zytC8uGbLNPUKrlciTg0w4ky16kYmpQ

Conclusion:

Thus, we have implemented a 4-bit UP DOWN counter using tinkercad.